

Lecture 4: Sensor interface circuits

■ Review of circuit theory

- Voltage, current and resistance
- Capacitance and inductance
- Complex number representations

■ Measurement of resistance

- Voltage dividers
- Wheatstone Bridge
- Temperature compensation for strain gauges

■ AC bridges

- Measurement of capacitance
- Measurement of impedance



Voltage, current, resistance and power

■ Voltage

- The voltage between two points is the energy required to move a unit of positive charge from a lower to a higher potential. Voltage is measured in Volts (V)

■ Current

- Current is the rate of electric charge through a point. The unit of measure is the Ampere or Amp (A)

■ Resistance

- Given a piece of conducting material connected to a voltage difference V , which drives through it a current I , the resistance is defined as

$$R = \frac{V}{I}$$

- As you will recall, this is known as **Ohm's Law**
- An element whose resistance is constant for all values of V is called an *ohmic* resistor
- Series and parallel resistors...

■ Power

- The power dissipated by a resistor is


$$P = VI = \frac{V^2}{R} = I^2R$$



Kirchhoff's Laws


■ 1st Law (for nodes)

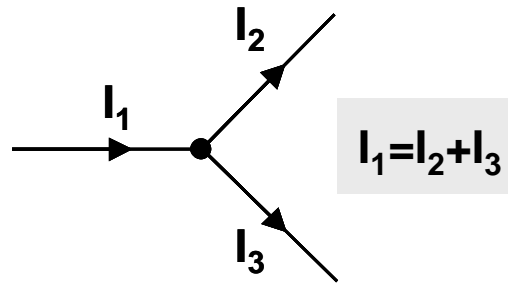- The algebraic sum of the currents into any node of a circuit is zero
 - Or, the sum of the currents entering equals the sum of the currents leaving
 - Thus, elements in series have the same current flowing through them



■ 2nd Law (for loops)

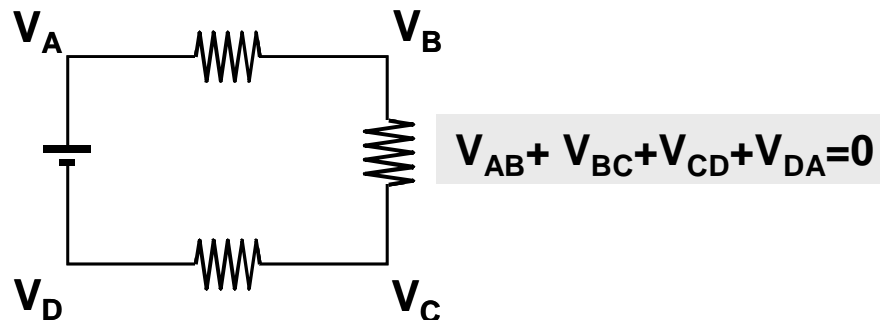- The algebraic sum of voltages in a loop is zero
 - Thus, elements in parallel have the same voltage across them.



Capacitors and inductors

- **A capacitor is an element capable of storing charge**

- The amount of charge is proportional to the voltage across the capacitor

$$Q = CV$$

- C is known as the capacitance (measured in *Farads*)
- Taking derivatives

$$\frac{dQ}{dt} = \frac{d(CV)}{dt} \Rightarrow I = C \frac{dV}{dt}$$

- Therefore, a capacitor is an element whose rate of voltage change is proportional to the current through it

- **Similarly, an inductor is an element whose rate of current change is proportional to the voltage applied across it**


$$V = L \frac{dI}{dt}$$

- L is called the inductance and is measured in Henrys



Frequency analysis

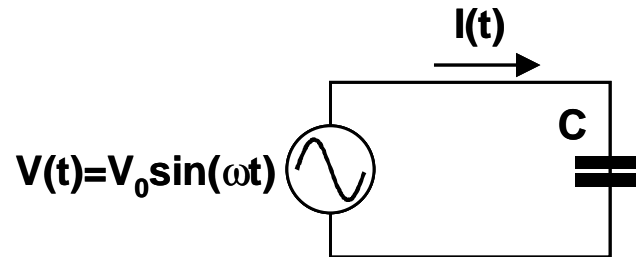- Consider a capacitor driven by a sine wave voltage



- The current through the capacitor is

$$I = C \frac{dV}{dt} = C \frac{d}{dt} (V_0 \sin(\omega t)) = C\omega V_0 \cos(\omega t)$$

- Therefore, the current phase-leads the voltage by 90° and the ratio of amplitudes is

$$\frac{|V(t)|}{|I(t)|} = \frac{1}{C\omega}$$


- What happens when the voltage is a DC source?



Voltages as complex numbers

- At this point it is convenient to switch to a complex-number representation of signals

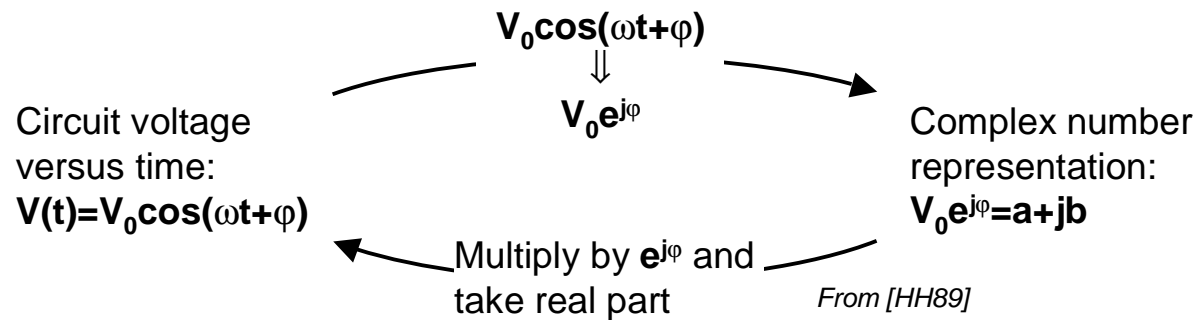- Recall that $e^{j\varphi} = \cos\varphi + j\sin\varphi$



- Applying this to the capacitor $V(t)/I(t)$ relationship

$$I = C \frac{dV}{dt} = C\omega V_0 \cos(\omega t)$$

$$\Downarrow$$

$$\frac{V}{I} = \frac{V_0 \sin(\omega t)}{C\omega V_0 \cos(\omega t)} = \frac{\cos(\omega t - \pi/2)}{C\omega e^{j0}} = \frac{e^{-j\pi/2}}{C\omega} = \frac{1}{C\omega e^{-j\pi/2}} = \frac{1}{j\omega C}$$



Impedance

- Impedance (Z) is a generalization of resistance for circuits that have capacitors and inductors

- Capacitors and inductors have **reactance**, while resistors have **resistance**

$$Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

$$Z_L = j\omega L$$

$$Z_R = R$$

- Ohm's Law generalized

$$\frac{V}{I} = Z$$

- Impedance in series and parallel

$$Z_S = Z_1 + Z_2 + \cdots + Z_N$$

$$\frac{1}{Z_P} = \frac{1}{Z_1} + \frac{1}{Z_2} + \cdots + \frac{1}{Z_N}$$




Example: High-pass filter

■ High pass filter

- The current through cap and resistor is
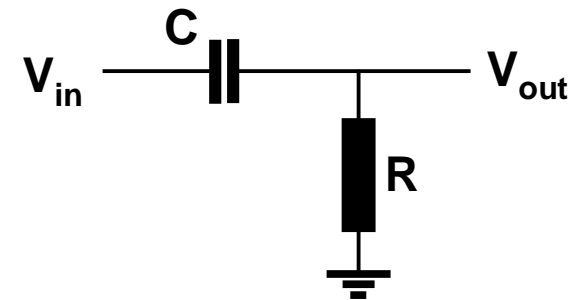
$$I = \frac{V_{in}}{Z} = \frac{V_{in}}{R + \frac{1}{j\omega C}}$$



- The output voltage is equal to the voltage differential across the resistor

$$V_{out} = RI = R \frac{V_{in}}{R + \frac{1}{j\omega C}}$$

- If we focus on amplitude and ignore phase

$$|V_{out}| = R \frac{|V_{in}|}{\left| R + \frac{1}{j\omega C} \right|} = R \frac{|V_{in}|}{\sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}} = |V_{in}| \frac{\omega RC}{\sqrt{(\omega RC)^2 + 1}}$$

- Asymptotic behavior...

- Corner frequency $\omega_{CORNER} = \frac{1}{RC} \Rightarrow 20 \log_{10} \frac{|V_{out}|}{|V_{in}|} = 20 \log_{10} \frac{1}{\sqrt{1+1}} = -3.010 \text{ dB}$



Measurement circuits

■ Resistance measurements

- Voltage divider (half-bridge)
- Wheatstone bridge

■ A.C. bridges

- Measurement of capacitance
- Measurement of impedance



Voltage divider

Assumptions



- Interested in measuring the fractional change in resistance x of the sensor: $R_S = R_0(1+x)$
 - R_0 is the sensor resistance in the absence of a stimuli
- Load resistor expressed as $R_L = R_0 k$ for convenience

The output voltage of the circuit is

$$\begin{aligned} V_{\text{out}} &= V_{\text{CC}} \frac{R_S}{R_S + R_L} = \\ &= V_{\text{CC}} \frac{R_0(1+x)}{R_0(1+x) + R_0 k} = V_{\text{CC}} \frac{1+x}{1+x+k} \end{aligned}$$

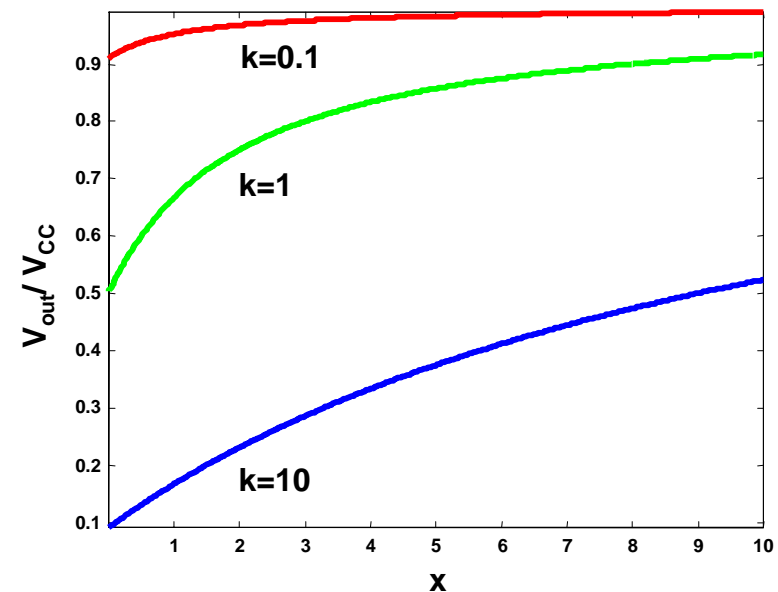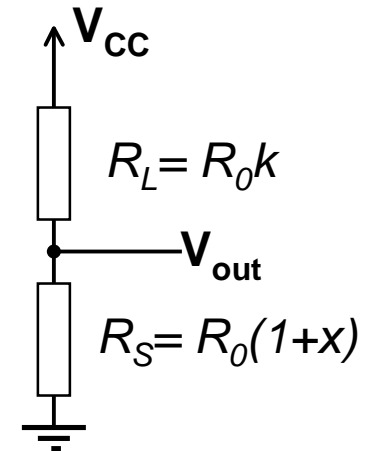Questions


- What if we reverse R_S and R_L ?
- How can we recover R_S from V_{out} ?



Voltage divider

- What is the sensitivity of this circuit?
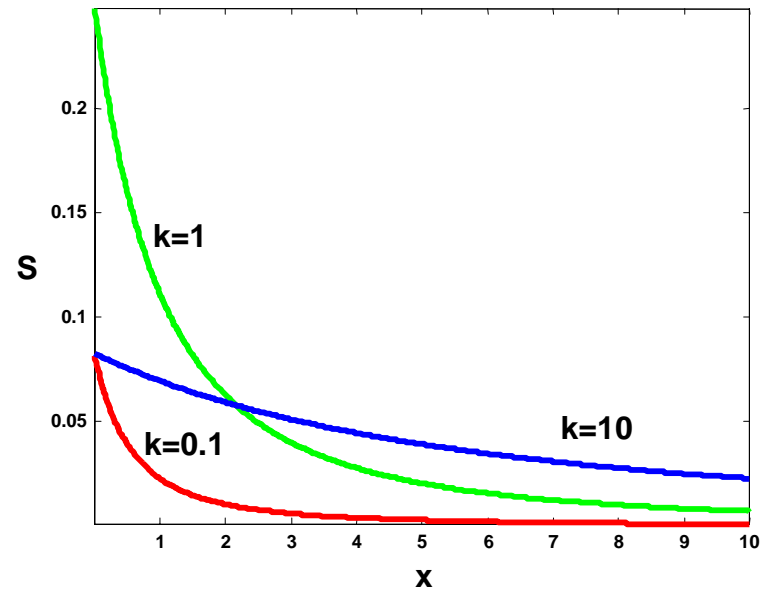
$$\begin{aligned} S &= \frac{dV_{\text{out}}}{dx} = \frac{d}{dx} \left(V_{\text{CC}} \frac{1+x}{1+x+k} \right) = \\ &= V_{\text{CC}} \frac{(1+x+k) - (1+x)}{(1+x+k)^2} = \\ &= V_{\text{CC}} \frac{k}{(1+x+k)^2} \end{aligned}$$



- For which R_L do we achieve maximum sensitivity?

$$\frac{dS}{dk} = 0 \Rightarrow \frac{d}{dk} \left(V_{\text{CC}} \frac{k}{(1+x+k)^2} \right) = 0 \Rightarrow \frac{(1+x+k)^2 - k2(1+x+k)}{(1+x+k)^2} = 0 \Rightarrow \mathbf{k = 1 + x}$$

- This is, the sensitivity is maximum when $R_L = R_S$



Wheatstone bridge

■ A circuit that consists of two dividers

- A reference voltage divider (left)
- A sensor voltage divider

■ Wheatstone bridge operating modes

- Null mode
 - R_4 adjusted until the balance condition is met:

$$V_{out} = 0 \Leftrightarrow R_3 = R_4 \frac{R_2}{R_1}$$


- Advantage: measurement is independent of fluctuations in V_{CC}

• Deflection mode

- The unbalanced voltage V_{out} is used as the output of the circuit

$$V_{out} = V_{CC} \left(\frac{R_3}{R_2 + R_3} - \frac{R_4}{R_3 + R_4} \right)$$

- Advantage: speed

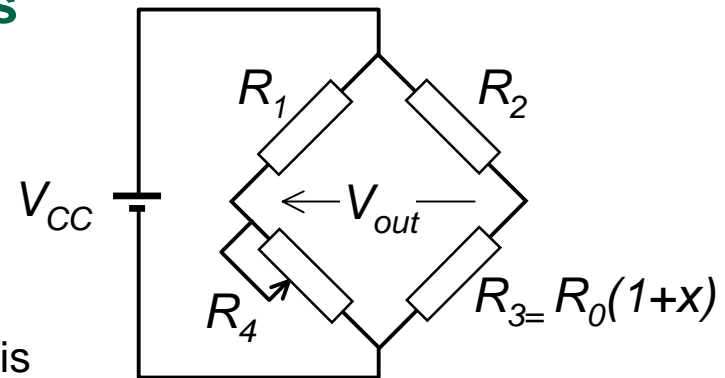


Wheatstone bridge

■ Assumptions

- Want to measure sensor fractional resistance changes $R_S=R_0(1+x)$
- Bridge is operating near the balance condition:
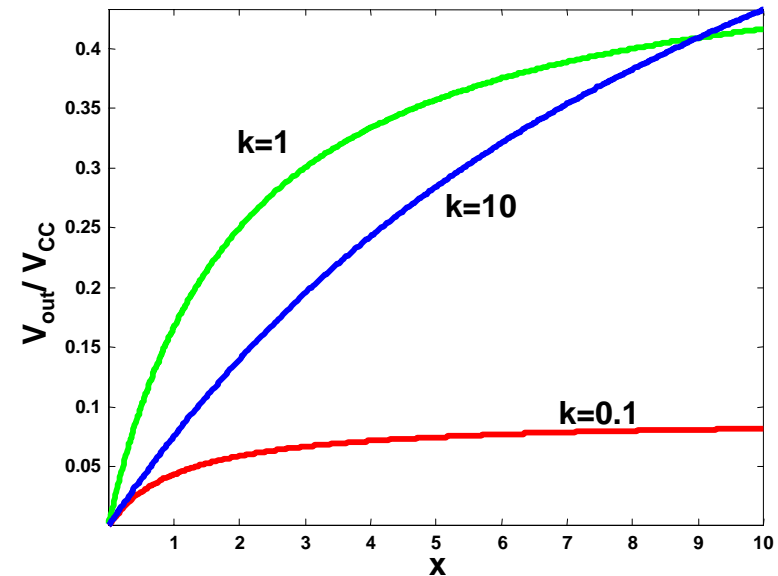
$$k = \frac{R_1}{R_4} = \frac{R_2}{R_0}$$



■ The output voltage becomes

$$\begin{aligned} V_{out} &= V_{CC} \left(\frac{R_0(1+x)}{R_0k + R_0(1+x)} - \frac{R_4}{R_4k + R_4} \right) = \\ &= V_{CC} \left(\frac{(1+x)}{k + (1+x)} - \frac{1}{k+1} \right) = V_{CC} \frac{kx}{(1+k)(1+k+x)} \end{aligned}$$



Wheatstone bridge

- What is the sensitivity of the Wheatstone bridge?


$$\begin{aligned} S &= \frac{dV_{\text{out}}}{dx} = V_{\text{CC}} \frac{d}{dx} \left(\frac{kx}{(1+k)(1+k+x)} \right) = \\ &= V_{\text{CC}} \frac{k(1+k)(1+k+x) - kx(1+k)}{(1+k)^2(1+k+x)^2} = \\ &= V_{\text{CC}} \frac{k}{(1+k+x)^2} \end{aligned}$$

- The sensitivity of the Wheatstone bridge is the same as that of a voltage divider
 - You can think of the Wheatstone bridge as a DC offset removal circuit
- So what are the advantages, if any, of the Wheatstone bridge?



Voltage divider vs. Wheatstone for small x



- The figures below show the output of both circuits for small fractional resistance changes
 - The voltage divider has a large DC offset compared to the voltage swing, which makes the curves look “flat” (zero sensitivity)
 - Imagine measuring the height of a person standing on top of a tall building by running a large tape measure from the street
 - The sensitivity of both circuits is the same!
 - However, the Wheatstone bridge sensitivity can be boosted with a gain stage
 - Assuming that our DAQ hardware dynamic range is 0-5VDC, $0 < x < 0.01$ and $k=1$, estimate the maximum gain that could be applied to each circuit

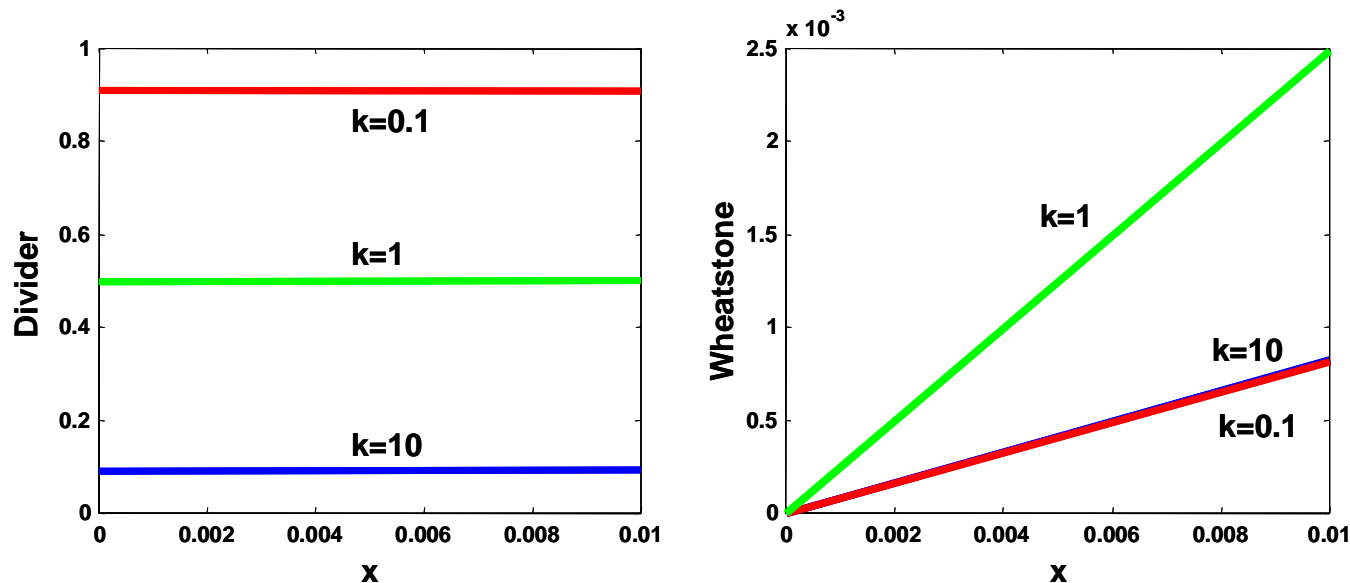

Compensation in a Wheatstone bridge

■ Strain gauges are quite sensitive to temperature

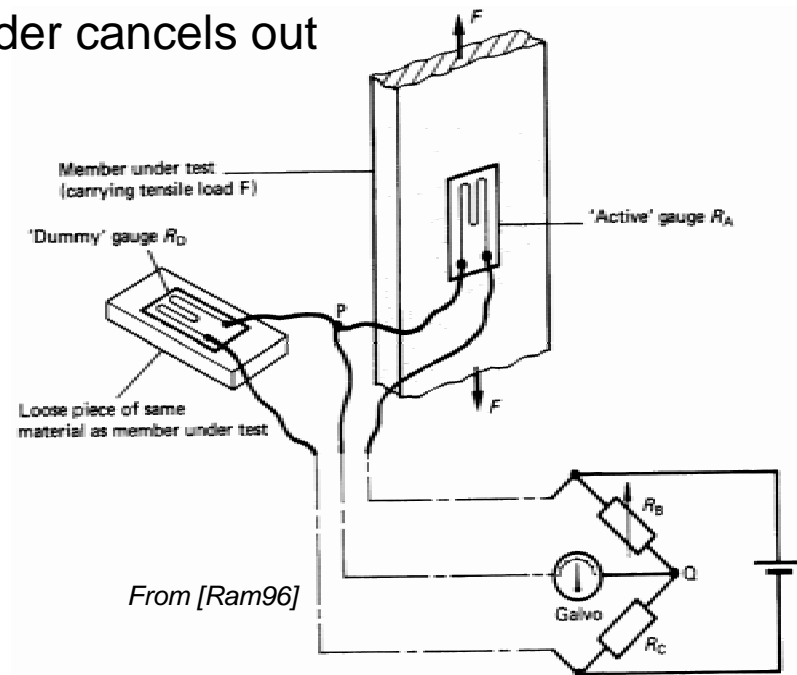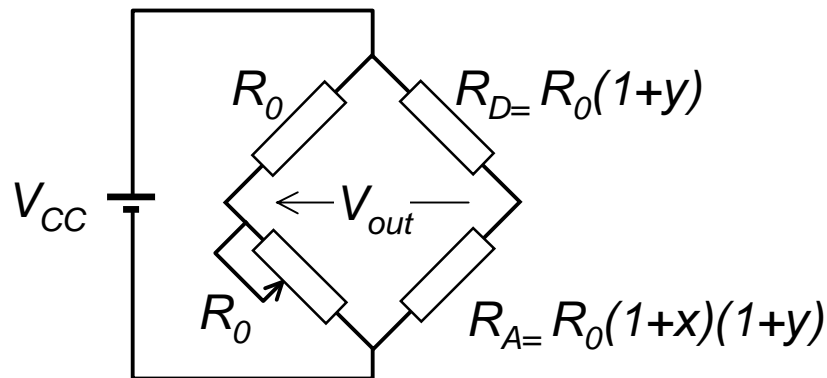- A Wheatstone bridge and a dummy strain gauge may be used to compensate for this effect
 - The “active” gauge R_A is subject to temperature (x) and strain (y) stimuli
 - The dummy gauge R_D , placed near the “active” gauge, is only subject to temperature
- The gauges are arranged according to the figures below
- The effect of $(1+y)$ on the right divider cancels out



AC bridges

- The structure of the Wheatstone bridge can be used to measure capacitive and inductive sensors

- Resistance replaced by generalized impedance
- DC bridge excitation replaced by an AC source

- The balance condition becomes

$$\frac{Z_1}{Z_4} = \frac{Z_2}{Z_3}$$


- which yields two equalities, for real and imaginary components

$$R_1R_3 - X_1X_3 = R_2R_4 - X_2X_4$$

$$R_1X_3 + X_1R_3 = R_2X_4 + X_2R_4$$

- There is a large number of AC bridge arrangements


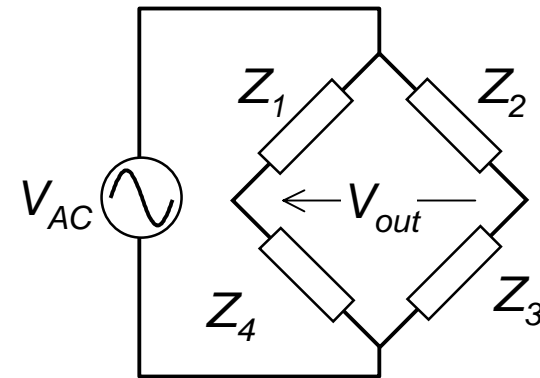
- These are named after their respective developer



AC bridges



■ Capacitance measurement

- Schering bridge
- Wien bridge

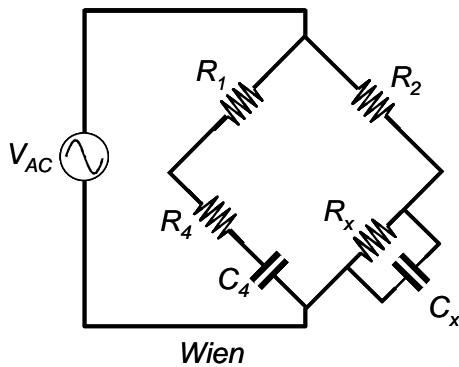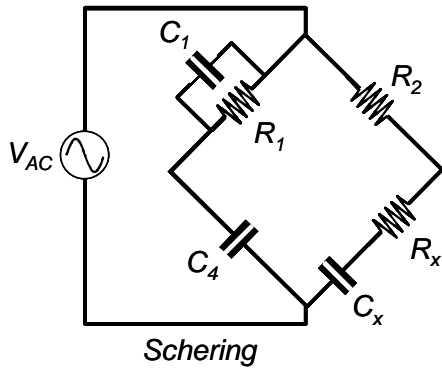

■ Inductance measurement

- Hay bridge
- Owen bridge

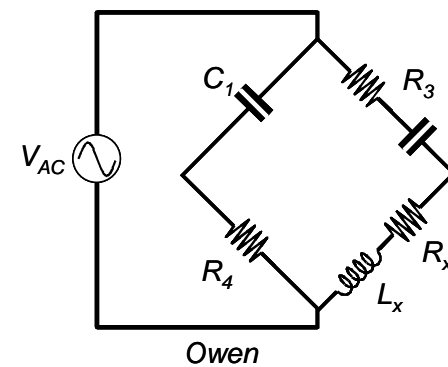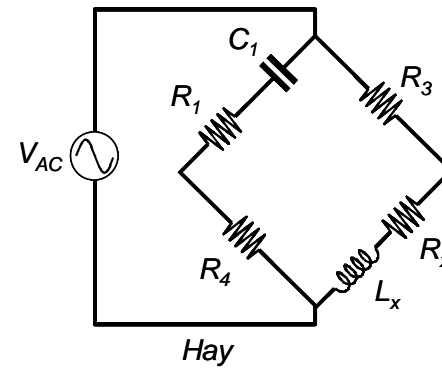

References

- [HH89] P. Horowitz and W. Hill, 1989, *The Art of Electronics*, 2nd Ed., Cambridge University Press, Cambridge, UK
- [Ram96] D. C. Ramsay, 1996, *Principles of Engineering Instrumentation*, Arnold, London, UK
- [Maz87] F. F. Mazda, 1987, *Electronic instruments and measurement techniques*, Cambridge Univ. Pr., New York
- [Die72] A. J. Diefenderfer, 1972, *Principles of electronic instrumentation*, W. B. Sanuders Co., Philadelphia, PA.
- [PAW91] R. Pallas-Areny and J. G. Webster, 1991, *Sensors and Signal Conditioning*, Wiley, New York
- [Gar94] J. W. Gardner, 1994, *Microsensors. Principles and Applications*, Wiley, New York.
- [Fdn97] J. Fraden, 1997, *Handbook of Modern Sensors. Physics, Designs and Applications*, AIP, Woodbury, NY

